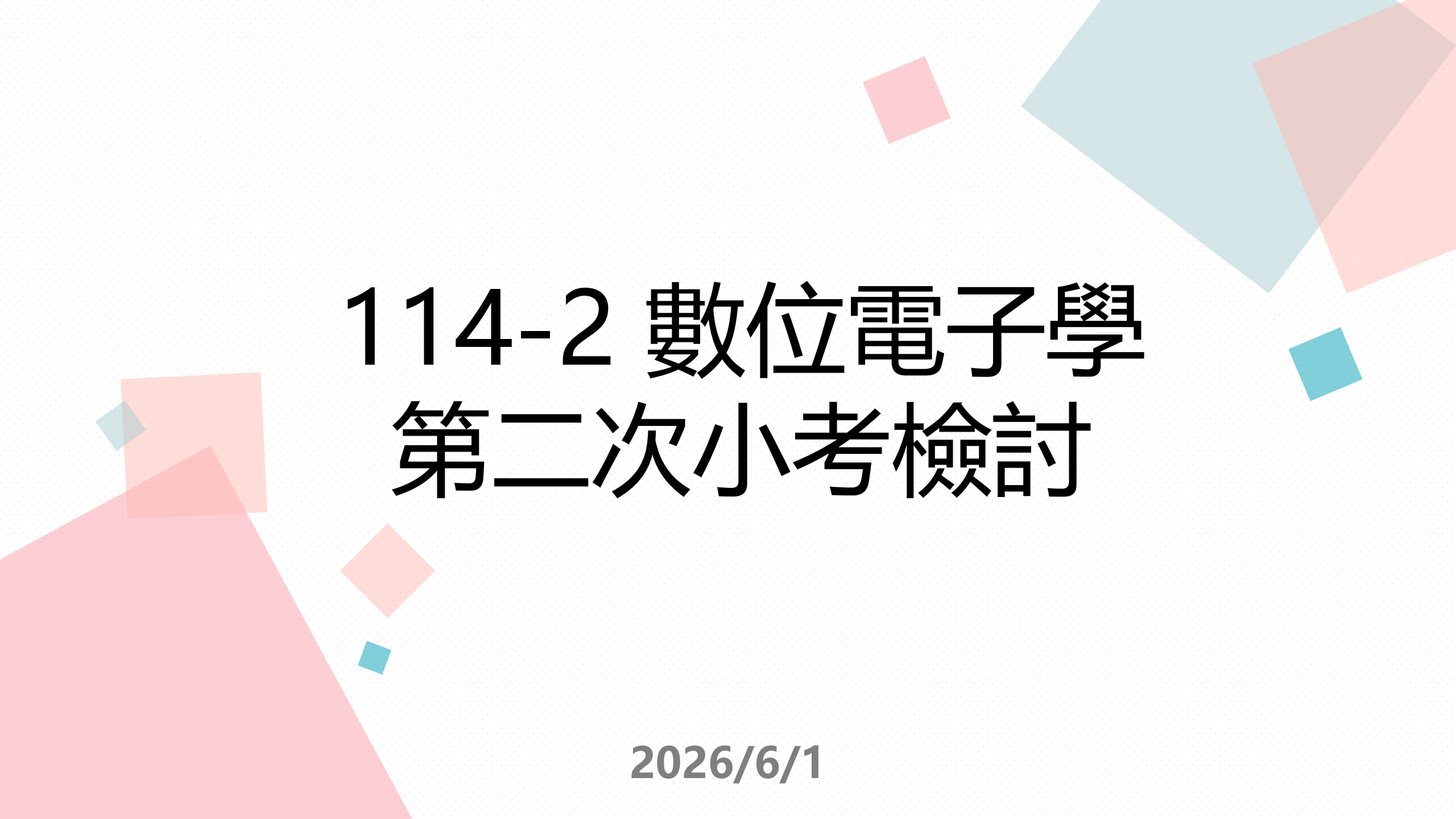




114-2 數位電子學 第二次小考檢討

2026/6/1

第一題

$$V_T = 25\text{mV}$$

$$V_{pb} = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$$

$$(1) N_A = 5 \times 10^{23}/\text{cm}^3, N_D = 3 \times 10^{19}/\text{cm}^3$$

$$V_{pb} = 2.5 \times 10^{-3} \ln\left(\frac{15 \times 10^{42}}{2.25 \times 10^{20}}\right)$$

$$V_{pb} = 2.5 \times 10^{-3} \ln\left(\frac{20}{3} \times 10^{22}\right) = 2.5 \times 10^{-3} \ln(6.67 \times 10^{22})$$

第一題

$$V_T = 25\text{mV}$$

$$V_{pb} = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$$

$$(2) N_A = N_D = 8 \times 10^{18}/\text{cm}^3$$

$$V_{pb} = 2.5 \times 10^{-3} \ln\left(\frac{64 \times 10^{36}}{2.25 \times 10^{20}}\right)$$

$$V_{pb} = 2.5 \times 10^{-3} \ln\left(\frac{256}{9} \times 10^{16}\right) = 2.5 \times 10^{-3} \ln(2.84 \times 10^{17})$$

第二題

- 截面積 $A = 300\text{mm}^2 = 3\text{cm}^2$
- 長度 $L = 2\text{cm}$
- 參雜濃度 $N_A = 5 \times 10^{15}/\text{cm}^3$
- 外加電壓 10V

$$\rho = \frac{1}{q N_A \mu_P} = \frac{1}{1.6 \times 10^{-19} \cdot 5 \times 10^{15} \cdot 450} = \frac{1}{0.36} (\Omega \cdot \text{cm})$$

$$R = \rho \cdot \frac{L}{A} = \frac{1}{0.36} \cdot \frac{2}{3} = \frac{50}{27} (\Omega) = 1.85(\Omega)$$

$$I = \frac{V}{R} = \frac{10}{\frac{50}{27}} = \frac{27}{5} (\text{A}) = 5.40(\text{A})$$


第三題

$$V_{CC} - V_{EB(ON)} - I_B R_B - V_{BB} = 0$$

$$20 - 0.7 - 15.9 I_B - 14 = 0$$

$$I_B = \frac{5.3}{15.9} = \frac{1}{3} \text{ (mA)}$$

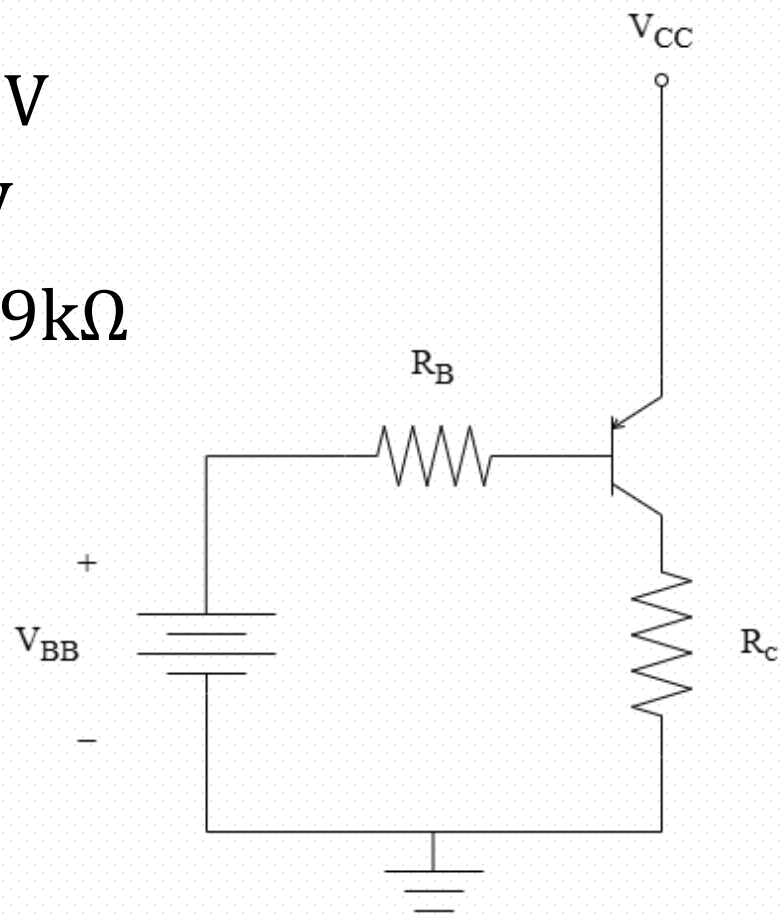- $V_{CC} = 20V$
- $V_{BB} = 6V$
- $R_B = 15.9k\Omega$



第三題

假設主動模式(act)：

$$I_C = \beta I_B$$


$$I_C = 100 \times \frac{1}{3} = \frac{100}{3} \text{ (mA)}$$

$$V_C = I_C R_C = \frac{100}{3} \times 6 = 200 \text{ (mA)}$$

$$V_E = V_{CC} = 20V$$

$$V_{EC} = 20 - 200 = -180 < 0.3 \dots (\times)$$

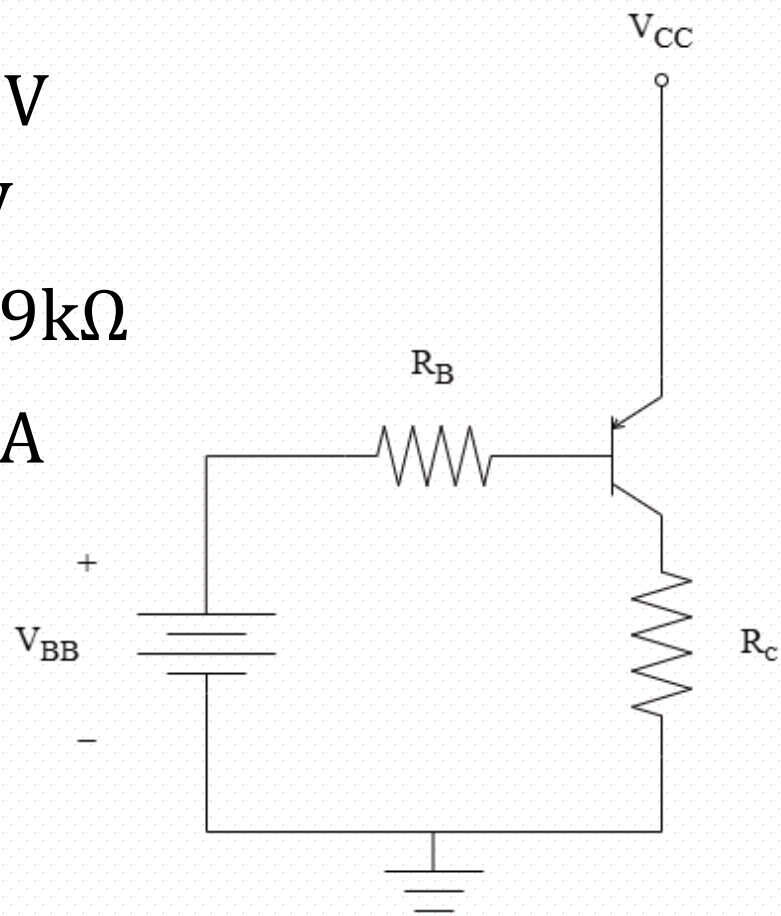- $V_{CC} = 20V$
- $V_{BB} = 6V$
- $R_B = 15.9k\Omega$
- $I_B = \frac{1}{3} \text{ mA}$



(1) $R_C = 6k\Omega$

第三題

假設飽和模式(sat)：


$$I_C = \frac{V_{CC} - V_{EC(SAT)}}{R_C} = \frac{20 - 0.2}{6} = 3.3(\text{mA})$$

(Check : $I_C < \beta I_B$)

$$I_E = I_C + I_B$$

$$I_E = 3.3 + \frac{1}{3} = 3.63(\text{mA})$$

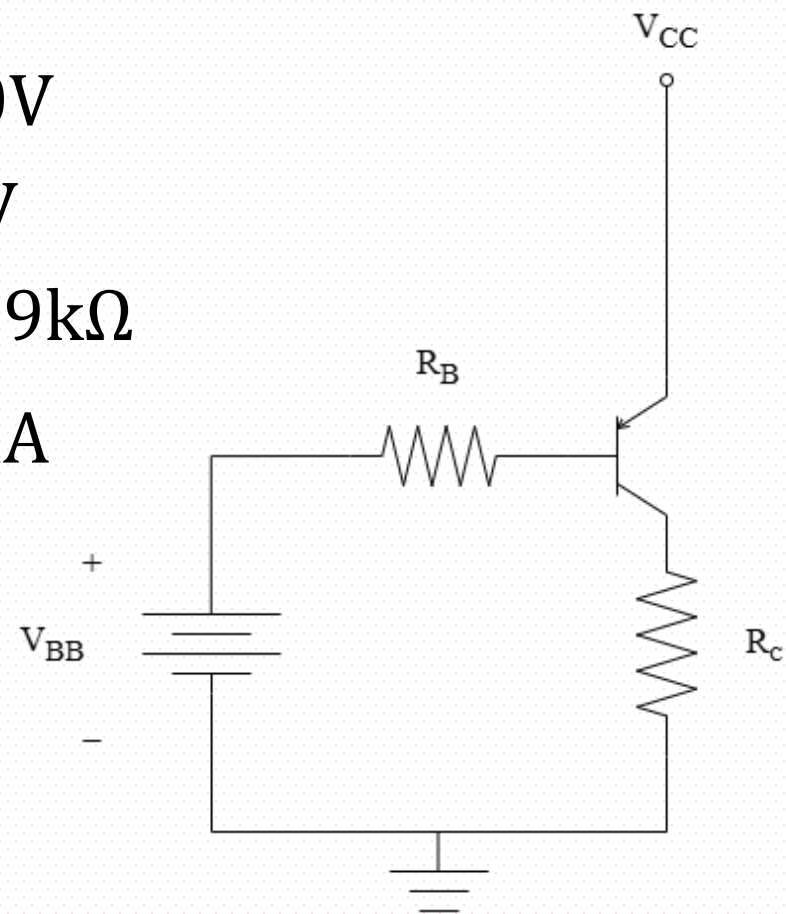- $V_{CC} = 20\text{V}$
- $V_{BB} = 6\text{V}$
- $R_B = 15.9\text{k}\Omega$
- $I_B = \frac{1}{3}\text{mA}$



(1) $R_C = 6\text{k}\Omega$

Ans :

$$I_C = 3.3\text{mA}$$

$$I_E = 3.63\text{mA}$$

第三題

假設主動模式(act)：

$$I_C = \beta I_B$$

$$I_C = 100 \times \frac{1}{3} = \frac{100}{3} \text{ (mA)}$$


$$V_C = I_C R_C = \frac{100}{3} \times 0.08 = 2.66 \text{ (mA)}$$

$$V_E = V_{CC} = 20V$$

$$V_{EC} = 20 - 2.66 = 17.33 > 0.3 \dots (\checkmark)$$

$$I_E = (\beta + 1) I_B = 33.67 \text{ (mA)}$$

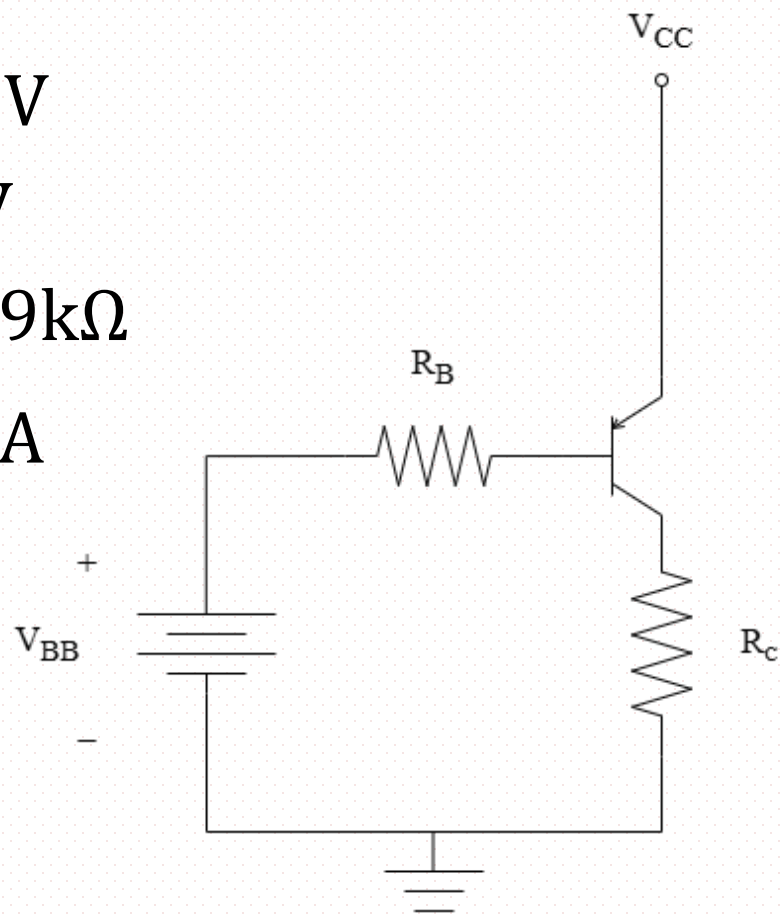- $V_{CC} = 20V$
- $V_{BB} = 6V$
- $R_B = 15.9k\Omega$
- $I_B = \frac{1}{3} \text{ mA}$



$$(2) R_C = 80\Omega$$

Ans :



$$I_C = \frac{100}{3} \text{ mA}$$

$$I_E = 33.67 \text{ mA}$$

第四題

$$V_{TH} = V_{CC} \times \frac{R_2}{R_1 + R_2} = 42 \times \frac{2}{2 + 2} = 21V$$

$$R_{TH} = R_1 // R_2 = 1(k\Omega)$$

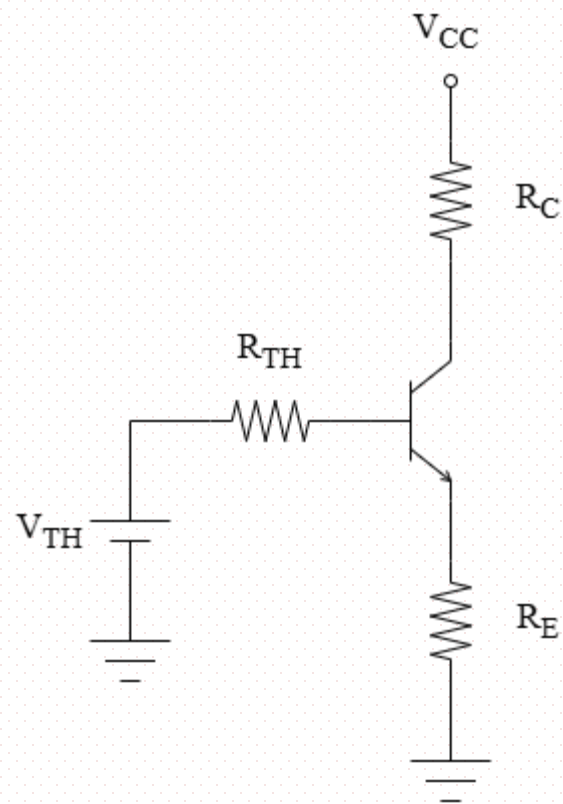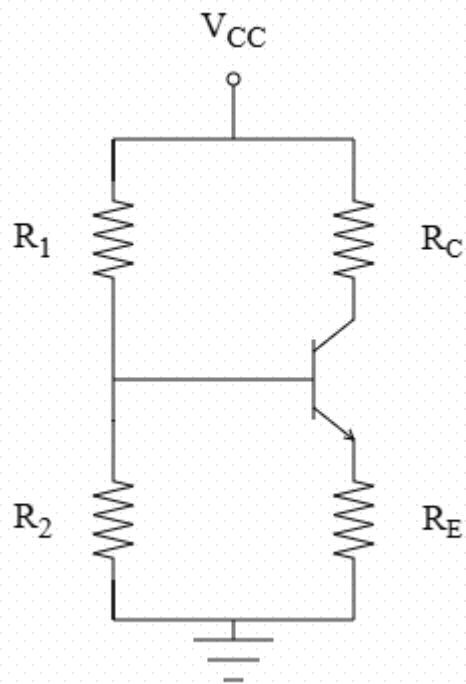

第四題

假設主動模式(act)：

$$V_{TH} - I_B R_{TH} - V_{BE(ON)} - I_E R_E = 0$$

$$21 - I_B - 0.7 - (101 \cdot I_B \cdot 2) = 0$$


$$20.3 = I_B \cdot 203$$

$$I_B = 0.1(\text{mA})$$

$$I_C = \beta I_B = 100 \times 0.1 = 10(\text{mA})$$

$$I_E = I_C + I_B = 10 + 0.1 = 10.1(\text{mA})$$

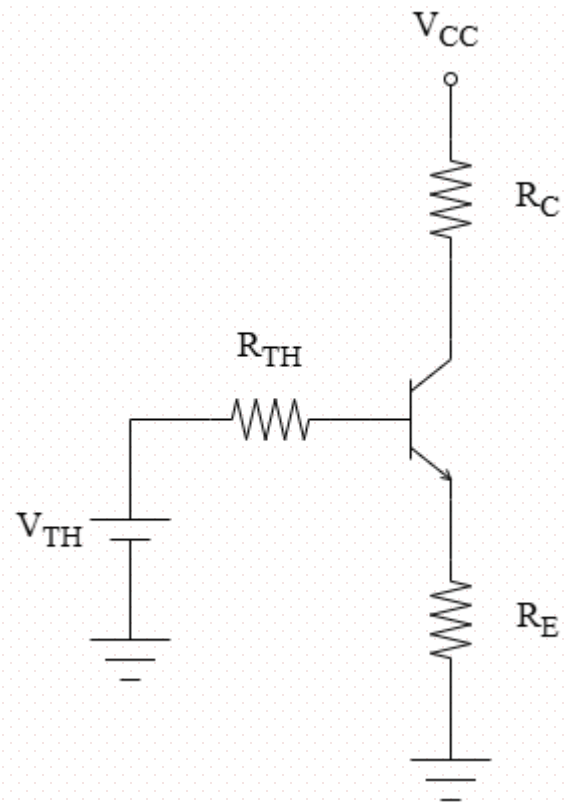- $V_{TH} = 21V$
- $R_{TH} = 1k\Omega$
- $R_C = 1k\Omega$
- $R_E = 2k\Omega$



第四題


- $V_{TH} = 21V$
- $R_{TH} = 1k\Omega$
- $R_C = 1k\Omega$
- $R_E = 2k\Omega$


$$V_E = I_E R_E = 10.1 \times 2 = 20.2V$$

$$V_C = V_{CC} - I_C R_C = 42 - (10 \times 1) = 32V$$

(check)

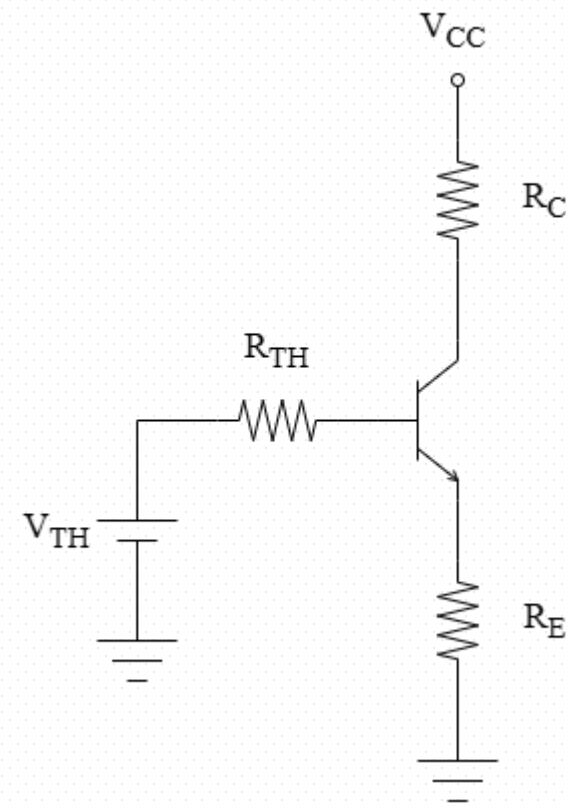
$$V_{CE} = V_C - V_E = 32 - 20.2 = 11.8 > 0.3 \dots (\checkmark)$$



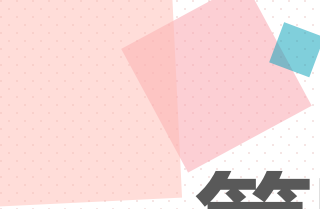

第四題_Ans

I_B	I_C	I_E	V_C	V_E
0.1mA	10mA	10.1mA	32V	20.2V

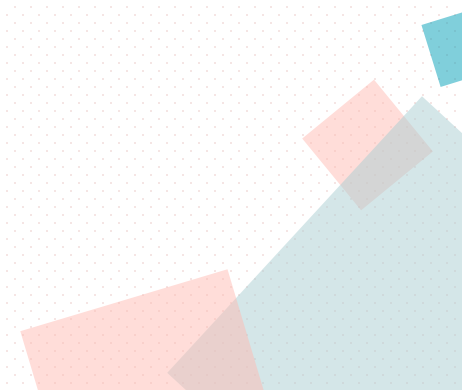

第五題

$$P = SI$$

$$300 = 5 \times I_C$$


$$I_C = 60(\text{mA})$$

V_x or V_y or $V_z = 16\text{V}$ 時，至少一 BJT 在飽和模式

$$V_{CC} - I_C R_C - V_D - V_{CE(\text{SAT})} = 0$$

$$8 - (60 \cdot R_C) - 3 - 0.2 = 0$$
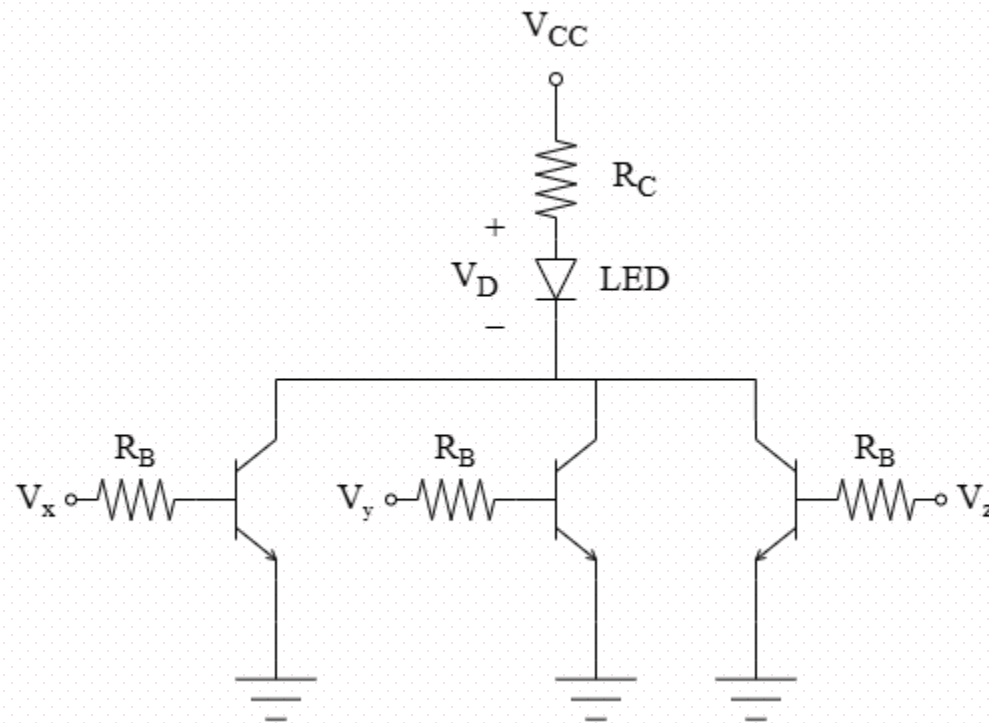
$$R_C = 0.08(\text{k}\Omega) = 80(\Omega)$$




第五題

題目 BJT 為並聯，LED 導通的條件是至少一個輸入為 16V

最佳情況：通三顆，每顆 BJT 只需 20mA

最差情況：通一顆，單獨一顆 BJT 需 60mA

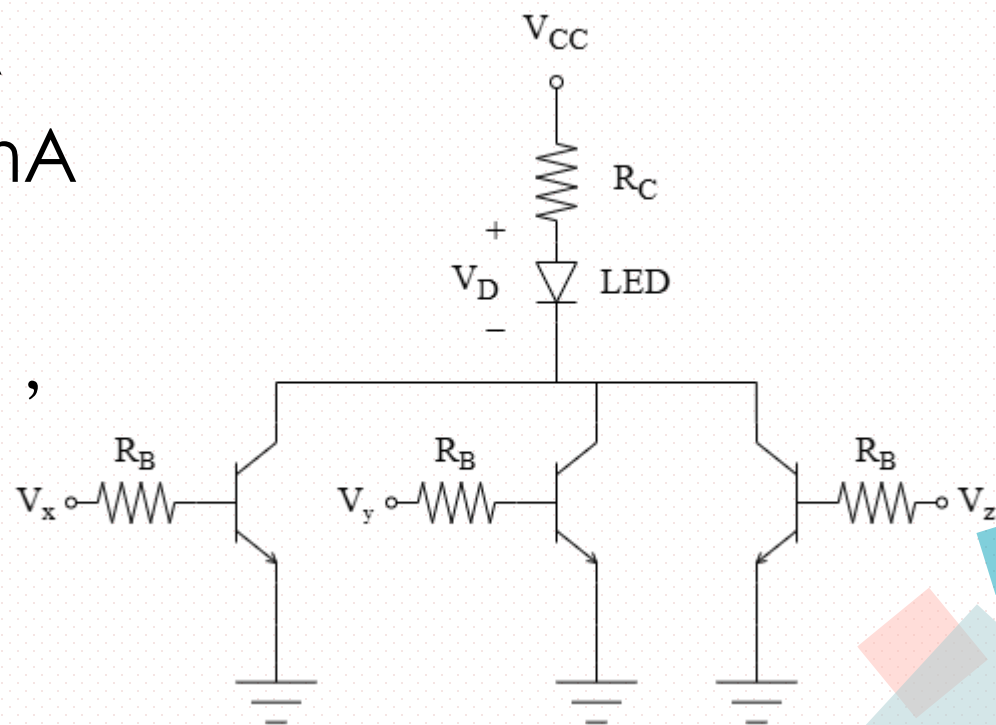要保證在最差情況下依然能進入飽和模式，
因此必須用 60mA 來推算所需的最小 I_B




第五題

$$I_C \leq \beta I_B$$

$$I_C \leq \beta \frac{V_X - V_{BE(ON)}}{R_B}$$

$$60 \leq 100 \cdot \frac{16 - 0.7}{R_B}$$

$$0.6 \leq \frac{15.3}{R_B}$$

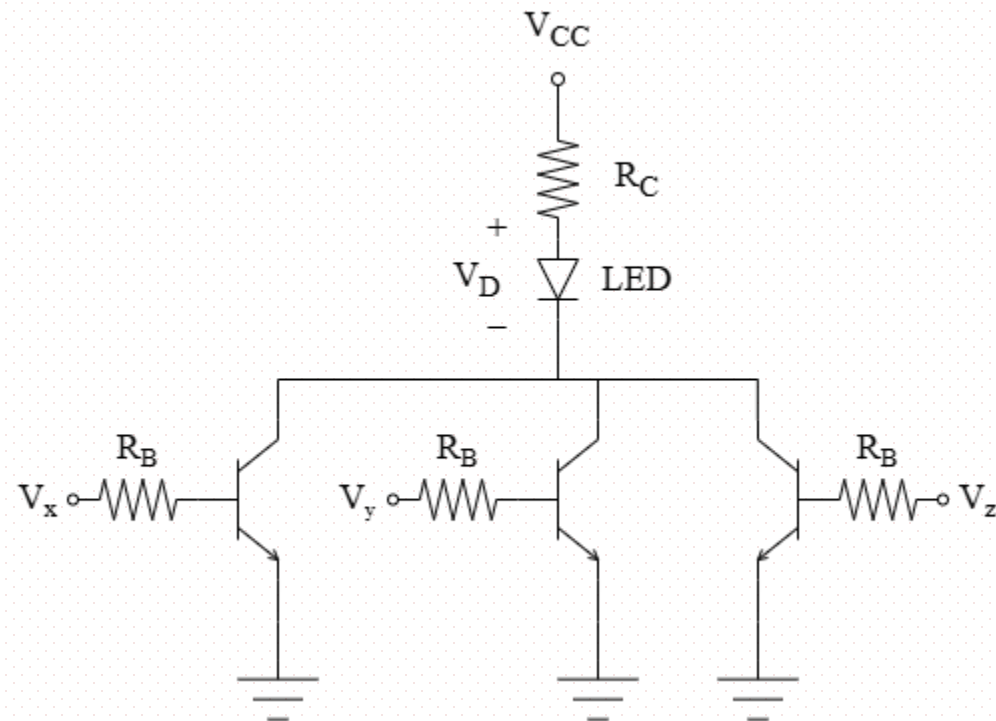

$$R_B \leq 25.5(\text{k}\Omega)$$

$$R_B = 25 (\text{k}\Omega)$$